

Lab2: Design a Postfix Calculator



National Chiao Tung University
Chun-Jen Tsai
9/25/2015

Lab 2: Design a Postfix Calculator


- ❑ In this lab, you will design a postfix calculator and use the ISE simulator to evaluate its correctness
 - The postfix calculator has an 4-bit input port that input a 4-bit operand or a 4-bit operator per clock cycle
 - The postfix calculator has an internal stack memory that stores operands and temporary results
 - The calculator only supports three operand $+$, $-$, \times
 - The expression has no more than 8 operands
- ❑ You will demo to your TA during the lab hours on 10/12
 - The testbench postfix_tb.v can be used to test your design

Postfix Expression

- ❑ In normal arithmetic expressions, we put operator in between two operands, for example, $2 + 7$. This is called infix expression
- ❑ For postfix expression, the operator is written behind the operands, for example, the infix expression " $2 + 7$ " is written as " $2\ 7\ +$ " in postfix notation
- ❑ For long expressions, postfix notation does not require parentheses for computation precedence, for example, " $(2 + 7) \times 5$ " can be written as " $2\ 7\ +\ 5\ \times$ "

Postfix Computation

 - ❑ A postfix expression is usually computed with the help of a stack storage using the following rules
 - If an operand is read from the input string, push it to the stack
 - If an operator is read from the input string, pop two operands from the stack and perform the computation, the result is push back to the stack
- ❑ For example, to compute $2\ 7\ +\ 5\ \times$



Module Specification (1/2)

- ❑ Module name: POSTFIX
- ❑ I/O ports:
 - Input ports: CLK, RESET, OP_MODE, IN_VALID, IN[3:0]
 - Output ports: OUT[15:0], OUT_VALID
- ❑ CLK is the clock signal for synchronous design
 - All signals are sampled at the positive edge of CLK
- ❑ RESET is the asynchronous, active low reset signal
- ❑ OP_MODE is high if IN[3:0] is an operator; low if IN[3:0] is an operand
- ❑ IN_VALID is high when IN[3:0] has valid input
 - High-to-low transition of IN_VALID signals the end of the input

Module Specification (2/2)

- ❑ When OP_MODE is high, the operator code of IN[3:0] is as follows:

IN[3:0] when OP_MODE == 1'b1	Operator
0001	+
0010	-
0100	×

- ❑ OUT[15:0] is a signed integer in two's complement
- ❑ OUT_VALID is high when the result is in OUT[15:0]
- ❑ OUT_VALID should go high in less than three cycles after IN_VALID becomes low

Timing Diagram

- ❑ The timing diagram of the sample input $2 \cdot 7 + 5 \cdot$ is as follows:

